

University of North Carolina at Charlotte
Department of Electrical and Computer Engineering
Laboratory Report 3
Network Analysis
Thevenin and Norton Equivalent Circuits
Time Constant of a RC Circuit

Laboratory Experiment Reports 8,9,10

Author: Patrick Hultberg

Lab Partner: Anthony Grancagnolo

Date: "12/1/2023"

1 Objectives

1.1 Network Analysis

The objective is to analyze a circuit and measure the real values to validate the calculated values.

1.2 Thevenin and Norton Equivalent Circuits

The objective of the lab is to utilize the Thevenin and Norton methods to calculate the current and voltage across any one of several resistors in a circuit and verify the calculated values by measuring the values in the circuits.

1.3 Time Constant of a RC Circuit

The objective is to measure the time constant of an RC circuit in order to verify the calculated values.

2 Equipment List

2.1 Network Analysis

- Digital Multimeter
- DC Power Supply
- Resistors: 470Ω , $1K\Omega$ (2), $5.1k\Omega$, $10k\Omega$

2.2 Thevenin and Norton Equivalent Circuits

- Digital Multimeter
- DC Power Supply
- Resistors: $1.2k\Omega$, $3.3k\Omega$, $10k\Omega$

2.3 Time Constant of a RC Circuit

- Digital Multimeter
- DC Power Supply
- Resistor: $20k\Omega$
- Capacitor: $2,200\mu F$
- Alligator (Clips) Jumper

3 Relevant Theory/Background Information

3.1 Network Analysis

In terms of relevant theory there is a wide variety of methods to calculate the current, voltage, and resistance across a circuit or individual elements. The primary base for all of these methods are Kirchoff's Voltage and Current laws which show the sum of the currents or voltages across a circuit will equal zero ergo:

$$0 = \sum_{i=1}^n V_i$$

and:

$$0 = \sum_{i=1}^n I_i$$

With the understanding of Kirchoff's Laws the methods of mesh current analysis, node voltage analysis, and superposition. When analysing using mesh current analysis the first step is to break a circuit into meshes which are smaller pieces of a circuit and are functionally the most basic circuit possible. Then apply Kirchoff's Voltage Law where the voltage across each resistor will be accounted for with Ohm's Law, $V = IR$, with current in resistors which are located in two loops the currents in each loop must be subtracted. Finally simply solve for each unknown element in each equation. When analysing using Node Voltage Analysis the first step is to selecting a node as reference or ground. Then use Kirchoff's Current Law for each node and repeat the process described previously. When utilizing Superposition the first step is to replace all but one current or voltage source with either an open circuit or short circuit respectively. Then apply whatever analysis functions best and repeat the process until all sources have been used. Finally sum all of the current and voltage values to solve for each respectively as seen here:

$$V = \sum_{i=1}^n V_i$$

and here:

$$I = \sum_{i=1}^n I_i$$

3.2 Thevenin and Norton Equivalent Circuits

Lorem ipsum dolor sit amet, consectetur adipiscing elit. Ut purus elit, vestibulum ut, placerat ac, adipiscing vitae, felis. Curabitur dictum gravida mauris. Nam arcu libero, nonummy eget, consectetur id, vulputate a, magna. Donec vehicula augue eu neque. Pellentesque habitant morbi tristique senectus et netus et malesuada fames ac turpis egestas. Mauris ut leo. Cras viverra metus rhoncus sem. Nulla et lectus vestibulum urna fringilla ultrices. Phasellus eu tellus sit amet tortor gravida placerat. Integer sapien est, iaculis in, pretium quis, viverra ac, nunc. Praesent eget sem vel leo ultrices bibendum. Aenean faucibus. Morbi dolor nulla, malesuada eu, pulvinar at, mollis ac, nulla. Curabitur auctor semper nulla. Donec varius orci eget risus. Duis nibh mi, congue eu, accumsan eleifend, sagittis quis, diam. Duis eget orci sit amet orci dignissim rutrum.

3.3 Time Constant of a RC Circuit

Lorem ipsum dolor sit amet, consectetur adipiscing elit. Ut purus elit, vestibulum ut, placerat ac, adipiscing vitae, felis. Curabitur dictum gravida mauris. Nam arcu libero, nonummy eget, consectetur id, vulputate a, magna. Donec vehicula augue eu neque. Pellentesque habitant morbi tristique senectus et netus et malesuada fames ac turpis egestas. Mauris ut leo. Cras viverra metus rhoncus sem. Nulla et lectus vestibulum urna fringilla ultrices. Phasellus eu tellus sit amet tortor gravida placerat. Integer sapien est, iaculis in, pretium quis, viverra ac, nunc. Praesent eget sem vel leo ultrices bibendum. Aenean faucibus. Morbi dolor nulla, malesuada eu, pulvinar at, mollis ac, nulla. Curabitur auctor semper nulla. Donec varius orci eget risus. Duis nibh mi, congue eu, accumsan eleifend, sagittis quis, diam. Duis eget orci sit amet orci dignissim rutrum.

4 Experimental Data/Analysis

4.1 Network Analysis

Table 8-1: Resistors Values

Resistance	Measured ($K\Omega$)	Color Code ($K\Omega$)	Error (%)
R_1	5.047k Ω	5.1k Ω	1.0392 %
R_2	467.5 Ω	470 Ω	.5319%
R_3	9.935k Ω	10k Ω	.65%
R_4	.999k Ω	1k Ω	.1%
R_5	.997k Ω	1k Ω	.3%

Table 8-2: Mesh Currents

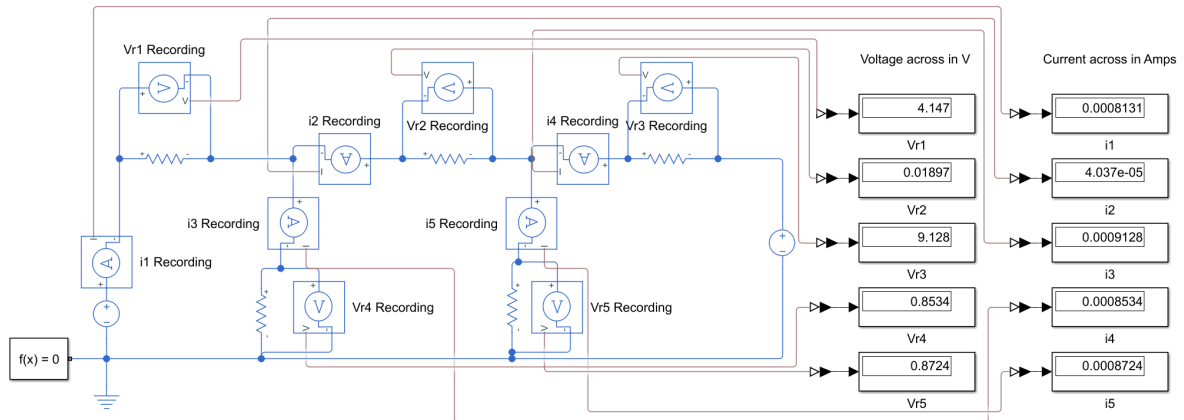
Current	Measured (mA)	Calculated (mA)	Error (%)
I_A	.806 mA	.813 mA	.861%
I_B	.043 mA	.0404 mA	5.581%
I_C	.910 mA	.913 mA	.329%

Table 8-3: Resistors Voltages

	Measured	Mesh Method	Nodal Analysis	Superposition	Simulation
V_{R1}	4.14 V	4.1463 V	4.43368 V	4.1466 V	4.147 V
V_{R2}	.021 V	.018988 V	.018 V	.01897 V	.01897 V
V_{R3}	9.123 V	9.13 V	9.128 V	9.158 V	9.128 V
V_{R4}	.852 V	.854 V	.853 V	.853 V	.8534 V
V_{R5}	.873 V	.8721 V	.872 V	.873 V	.8724 V

Table 8-4: Resistors Current

	Measured	Mesh Method	Nodal Analysis	Superposition	Simulation
I_{R1}	.803 mA	.813 mA	.8131 mA	.81305 mA	.8131 mA
I_{R2}	.043 mA	.0406 mA	.0404 mA	.04037 mA	.04034 mA
I_{R3}	.911 mA	.913 mA	.9128 mA	.91276 mA	.9128 mA
I_{R4}	.825 mA	.8536 mA	.853 mA	.853 mA	.8534 mA
I_{R5}	.834 mA	.8271 mA	.872 mA	.873 mA	.8724 mA

**Figure 8-2: Simulated model of the circuit in Figure 8-1**

4.2 Thevenin and Norton Equivalent Circuits

Table 9-1: Calculated Voltage and Current for Resistor R3

	Thevenin Equivalent	Norton Equivalent
I_{R3}	4.9 mA	4.9 mA
V_{R3}	16.17 V	16.17 V

Table 9-2: Measured Thevenin and Norton Equivalents

Thevenin Equivalent		Norton Equivalent	
v_{TH}	21.43 V	i_N	18.3 mA
R_{TH}	1.056k Ω	R_N	1.056k Ω

Table 9-3: Measured Voltage and Current for Resistor R3

	Figure 9-3	Thevenin Equivalent	Norton Equivalent
I_{R3}	4.961 mA	4.961 mA	4.596 mA
V_{R3}	16.19 V	16.18 V	15 V

4.3 Time Constant of a RC Circuit

Table 10-1: Data Table for RC Time Constant

Time (min:sec)	Current (mA)			Resistor Volt- age (V)	Capacitor Voltage (V)
	Trial 1	Trial 2	Average		
0:00	1.745 mA	1.745 mA	1.745 mA	34.9 V	0 V
0:15	1.242 mA	1.24 mA	1.241 mA	24.82 V	10.08 V
0:30	.901 mA	.900 mA	.9005 mA	18.01 V	16.86 V
0:45 τ	.662 mA	.666 mA	.664 mA	13.28 V	21.62 V
1:00	.490 mA	.500 mA	.495 mA	9.9 V	25 V
1:15	.365 mA	.373 mA	.369 mA	7.38 V	27.52 V
1:30	.277 mA	.274 mA	.2755 mA	5.51 V	29.39 V
1:45	.212 mA	.207 mA	.2095 mA	4.19 V	30.71 V
2:00	.165 mA	.158 mA	.1615 mA	3.23 V	31.67 V
2:15	.125 mA	.112 mA	.1185 mA	2.37 V	32.53 V
2:30	.100 mA	.092 mA	.096 mA	1.92 V	32.98 V
2:45	.076 mA	.072 mA	.074 mA	1.48 V	33.42 V
3:00	.062 mA	.057 mA	.0595 mA	1.19 V	33.71 V
3:15	.050 mA	.045 mA	.0475 mA	.95 V	33.95 V
3:30	.041 mA	.036 mA	.0385 mA	.77 V	34.13 V
3:45	.034 mA	.029 mA	.0315 mA	.63 V	34.27 V
4:00	.028 mA	.024 mA	.026 mA	.52 V	34.38 V
4:15	.023 mA	.020 mA	.0215 mA	.43 V	34.47 V
4:30	.020 mA	.016 mA	.018 mA	.36 V	34.54 V
4:45 5τ	.017 mA	.014 mA	.0155 mA	.31 V	34.59 V
5:00	.015 mA	.012 mA	.0135 mA	.27 V	34.63 V
5:15	.013 mA	.010 mA	.0115 mA	.23 V	34.67 V
5:30	.011 mA	.009 mA	.010 mA	.2 V	34.7 V
5:45	.010 mA	.008 mA	.009 mA	.18 V	34.72 V
6:00	.009 mA	.007 mA	.008 mA	.16 V	34.74 V

5 Conclusions

5.1 Network Analysis

Each method of calculation will introduce error due to its assumption of ideal conditions. Furthermore, each almost all methods of calculations will give similar value but will vary in precision.

5.2 Thevenin and Norton Equivalent Circuits

Thevenin and Norton equivalent circuits are way to reduce circuits to a simpler form that makes finding current though, voltage in, and resistance in a circuit. The Norton Current and Thevenin Voltage will be the values across the load resistor. Norton Resistance equals Thevenin Resistance and the Thevenin Voltage is equal to the Thevenin Resistance times the Norton Current.

5.3 Time Constant of a RC Circuit

As a capacitor is charged current will decrease until the capacitor is fully charged thus making an open circuit. Furthermore, the voltage will be collected into the capacitor as the voltage across the resistor goes down.

6 Post Lab

6.1 Network Analysis

1. From the data obtained in this experiment, calculations and simulations; discuss on the validity of Mesh Analysis, Nodal Analysis, and superposition.

Depending on the precision required to measure the voltage and current will result in each method being more or less accurate. Those which require more precision in the measure of voltage will mean that the the node method is more accurate whereas in the case of current the loop method is more accurate.

6.2 Thevenin and Norton Equivalent Circuits

1. From the data obtained in this experiment and prelab calculations simulations; discuss on
 - (a) Observations regarding the current through resistor R3.
 - (b) Observations regarding the voltage across resistor R3.
 - (c) Observations regarding the Thevenin equivalent.
 - (d) Observations regarding the Norton equivalent.

6.3 Time Constant of a RC Circuit

1. From the data obtained in this experiment in a single graph;
 - (a) Plot V_R vs. time
 - (b) Plot V_c vs. time
2. After the graphs have been completed, do the following:
 - (a) Describe the capacitor voltage behavior from 0 through 5τ , in terms of initial and final voltage magnitude, linearity and rate of change.
 - (b) Describe the resistor voltage behavior from 0 through 5τ , in terms of initial and final voltage magnitude, linearity and rate of change.
 - (c) To how many volts has V_c charged in one time constant?
 - (d) To what % has the capacitor charged to at this point?
 - (e) Using the equation in the introduction section of this experiment, show the calculation of V_c for a time equal to one time constant.
 - (f) How many volts are across the resistor at the end of one time constant? What % is this of the total possible voltage change?
 - (g) From the graphs read the values of capacitor and resistor voltage at 4 minutes.
 - (h) Calculate the values of capacitor and resistor voltage at 4 minutes.
 - (i) From the results of g and h above, what do you conclude about the accuracy of your graphs?